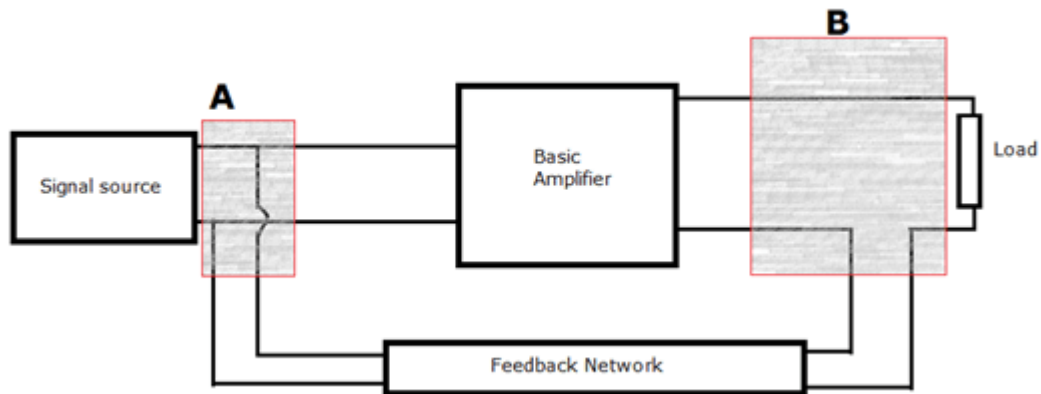


Objective Questions

- Physical or logical arrangement of network is _____
 - a) Topology
 - b) Routing
 - c) Networking
 - d) Control
- In the following diagram, shaded portions are named A and B.



What are A and B?

- a) A = Current sampling network, B = Voltage sampling network
 - b) A = Current mixing network, B = Voltage sampling network
 - c) A = Shunt mixing network, B = Current sampling network
 - d) A = Voltage mixing network, B = Current sampling network
- Voltage shunt feedback amplifier forms
 - a) A negative feedback
 - b) A positive feedback
 - c) Both positive and negative
 - d) None of the mentioned
 - Voltage shunt feedback amplifiers are also called as
 - a) Non-inverting amplifier with feedback
 - b) Non-inverting amplifier without feedback
 - c) Inverting amplifier with feedback
 - d) Inverting amplifier without feedback
 - In a voltage-series feedback topology, the feedback signal is taken from:
 - a) The output voltage
 - b) The input voltage
 - c) The output current
 - d) The input current

- Which feedback topology is commonly used in operational amplifiers (op-amps)?
 - a) Voltage-series feedback
 - b) Current-series feedback
 - c) Voltage-shunt feedback
 - d) Current-shunt feedback
- In voltage-shunt feedback, the feedback signal is applied to:
 - a) The input voltage
 - b) The output voltage
 - c) The input current
 - d) The output current
- Which feedback topology tends to have a lower output impedance?
 - a) Voltage-series feedback
 - b) Current-series feedback
 - c) Voltage-shunt feedback
 - d) Current-shunt feedback
- A feedback circuit usually employs network
 - a) Resistive
 - b) Capacitive
 - c) Inductive
 - d) None of the above
- _____ are the disadvantages of positive feedback.
 - a) Instability
 - b) Increasing distortion
 - c) All of the above
 - d) None of the above

Answers

1-a,2-c,3-a,4-c,5-a,6-a&c,7-a,8-b,9-a ,10-c